

# EECS 247


## Lecture 14: Pipelined ADCs Figures of Merit and Trends

# Today's Lecture

- Pipelined ADCs
  - Combining the bits
  - Stage implementation
    - Circuits
    - Noise budgeting
- Figures of Merit and Trends
  - How to use/not use FOMs
  - FOMs over time

# Combining the Bits

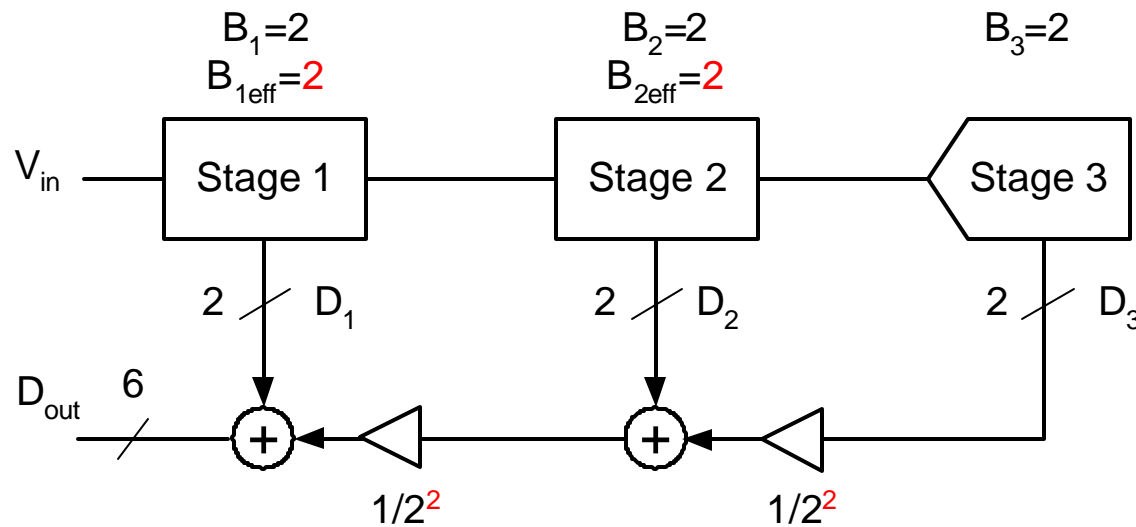- Example: Three 2-bit stages, no redundancy




$$D_{out} = D_1 + \frac{1}{4} D_2 + \frac{1}{16} D_3$$
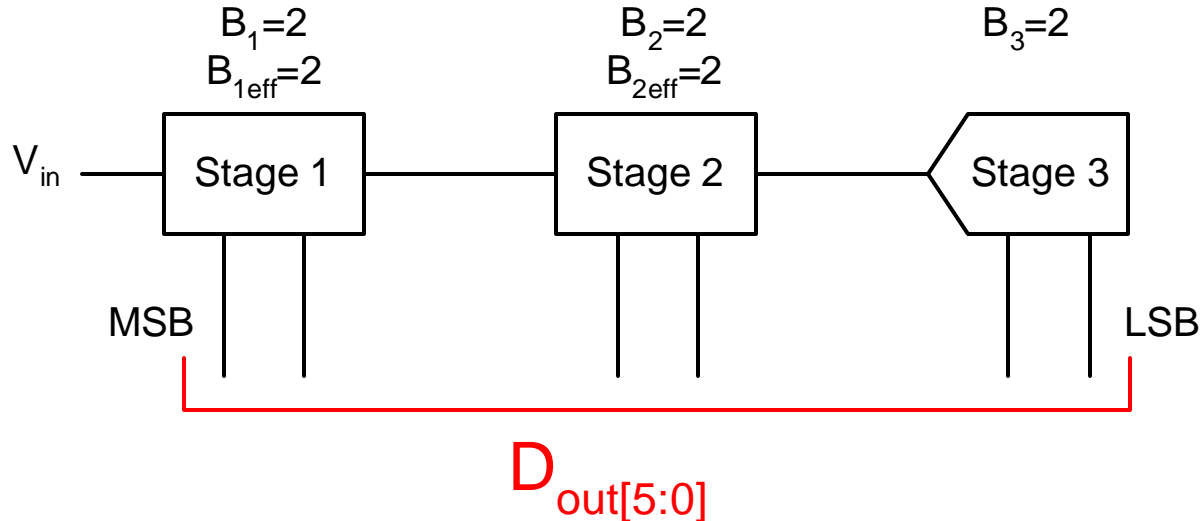
# Combining the Bits


$D_1$     **XX**  
 $D_2$         **XX**  
 $D_3$             **XX**  
-----  
 $D_{out}$     **DDDDDD**

- Only bit shifts
- No arithmetic circuits needed



# Combining the Bits

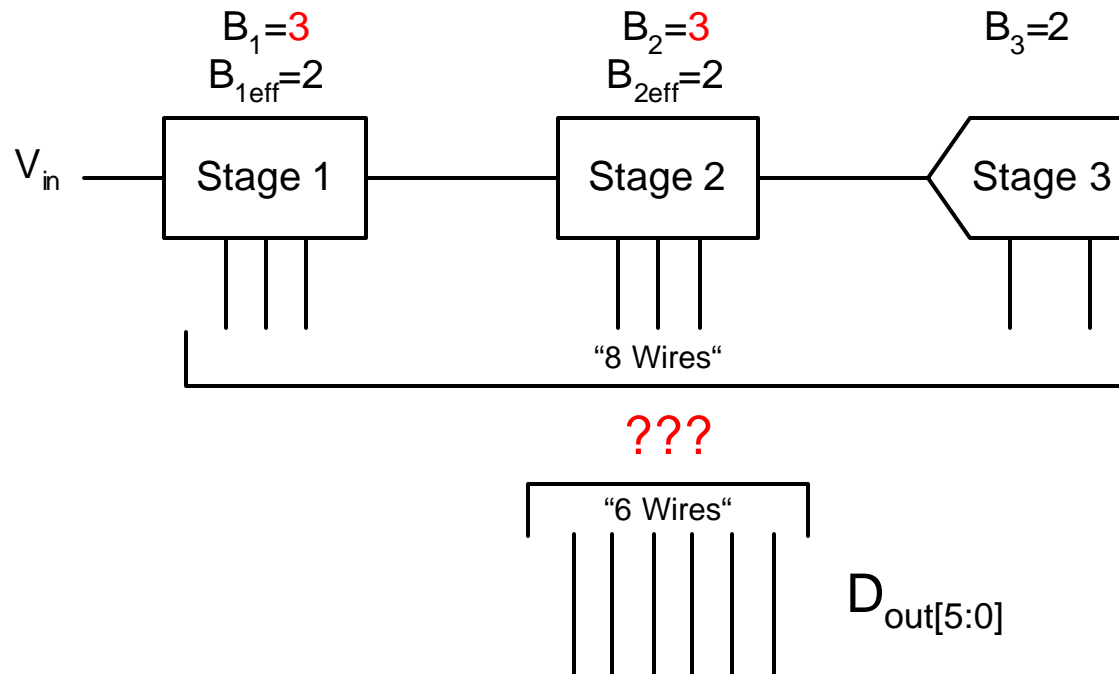- Example: Three 2-bit stages, one bit redundancy in stages 1 and 2




# Combining the Bits

$$D_{out} = D_1 + \frac{1}{4}D_2 + \frac{1}{16}D_3$$



- Bits overlap
- Need adders

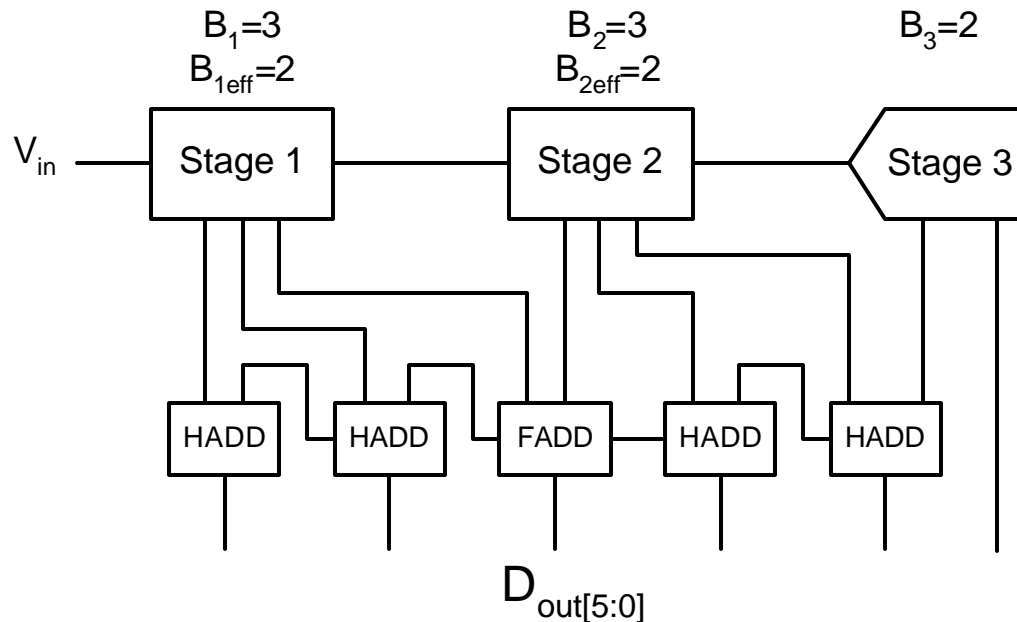

以上内容仅为本文档的试下载部分，为可阅读页数的一半内容。如要下载或阅读全文，请访问：<https://d.book118.com/625324113212011213>